

A Zener Diode tester

Zener diodes are a common cause of faults in electronic equipment, so it's helpful to have a means of checking them. This simple meter, devised by **Michael Dranfield**, is a useful addition to your test armoury


Unlike most semiconductor devices, zener diodes cannot be checked with a multimeter. A zener diode may seem to be OK when forward biased, but may stabilise at the wrong voltage or not at all. We recently had a Samsung SI3240 VCR in with tuning problems, and found that the voltage across the 33V stabilising device was only 25V. In this case the cause of the problem was easy to diagnose, and there was no other damage. Things can be more tricky when the faulty zener diode is part of a switch-mode power supply: the whole power supply might blow up at switch on, especially where DC coupling is used throughout. We've had this happen with the Ferguson FV31 VCR and ICC5 chassis.

The tester described in this article applies a current-limited, high-voltage supply across the zener diode under test, showing the breakdown voltage on a liquid-crystal display with an accuracy of 0.1V.

Circuit Description

The circuit of the tester is shown in Fig. 1. It employs a single-transistor oscillator that runs at approximately 3kHz. Mains transformer T1 is used in reverse: its centre-tapped 4.5-0-4.5V winding is the oscillator transistor's load, the 0-240V winding stepping up the voltage to feed bridge rectifier BR1. When pushbutton switch PB1 is pressed, a voltage starts to build up across the rectifier's reservoir capacitor C4. This build up continues until the zener diode being tested starts to conduct. The conduction point is the diode's zener breakdown voltage, and is displayed directly by the LCD panel. R2 limits the current flowing through the diode to about 5mA.

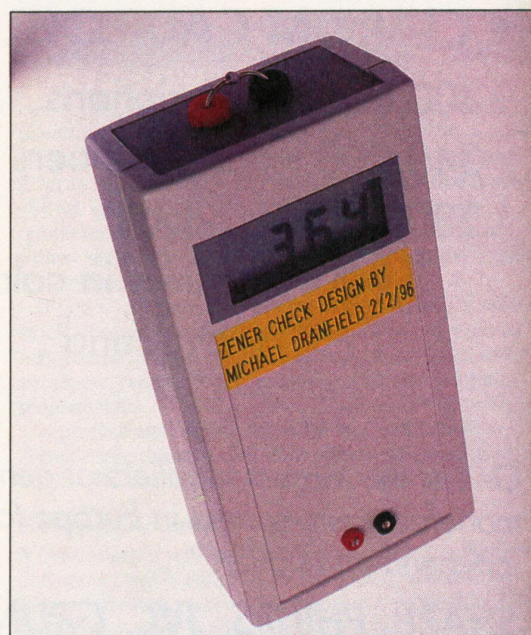The display device is a digital LCD voltmeter module that's available from Maplin. It has a maximum read out of 199.9V, which is not a problem since zener diodes with a higher breakdown voltage are rarely used. R3 and R4 calibrate the meter: the LCD module has a built-in preset for fine adjustment.



Approximately 350V is developed across C4. If the unit is run without a zener diode in circuit the display will over-range, displaying a one. No damage will be done to the display, but if you wish you can limit the test voltage at approximately 200V by connecting a 1.2M Ω resistor across C4.

Construction

Circuit layout is not critical. I etched my own board, but you could build the unit using tagstrip or Veroboard. The prototype unit is housed in a very professional-looking instrument case with a display window and a PP3 battery compartment. The case costs about £8 + VAT from Farnell while the Maplin GW01B display unit costs £11.95.

Setting Up

Initial setting up is easy. Insert a known good zener diode with a breakdown voltage of say 9.1V. Connect a digital multimeter across the zener diode. Switch on and adjust the preset on the LCD panel so that the reading is exactly the same as that displayed by the multimeter. Don't rely on the zener diode alone for calibration, as most zener diodes have a $\pm 5\%$ tolerance and the breakdown voltage can also vary with temperature.

In view of the high voltage present, in-circuit testing is not recommended. Although the input impedance is very high, touching the test terminals with your finger could still make you jump!

Use

Insert the suspect zener diode in the test socket. Push the button and hold it for a few seconds, until the reading stabilises. This is the diode's working voltage. If the meter reads 0.7V the zener diode is connected the wrong way round, with forward bias applied.

Happy testing!

Components required

Tr1	2SC1815
C1	100µF, 25V
C2	0.047µF, 250V polyester
C3	0.047µF, 250V polyester
C4	2.2µF, 400V
BR1	400V, 1A bridge rectifier
R1	10kΩ
R2	10kΩ
R3	4.7MΩ
R4	4.7kΩ
T1	Farnell 432-684
PB1	Farnell 140-690 miniature pushbutton switch
LCD	Maplin GW01B digital LCD voltmeter
Case	Farnell 465-963
Test sockets Farnell 145-299 (red), 145-300 (black).	
PP9 battery.	

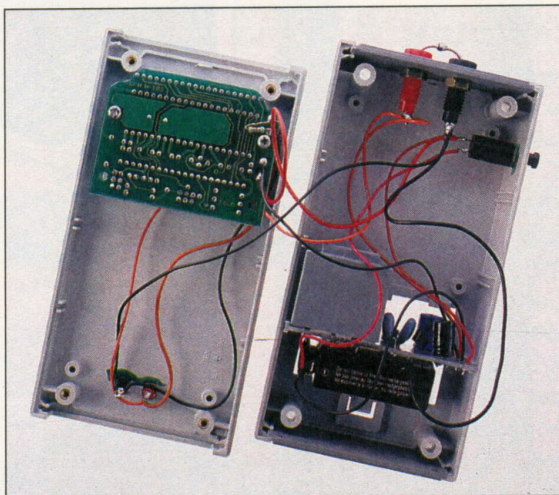
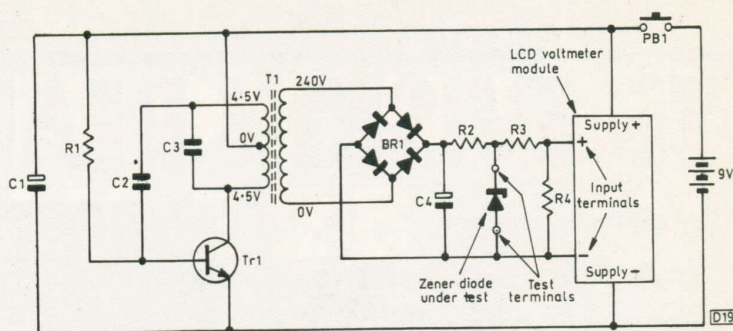


Fig. 1: Circuit diagram of the tester. Do not connect the negative side of C4 to the battery's negative terminal, as the LCD panel won't work in this condition.

JJ's SUMMER SIZZLERS

HURRY - HURRY TILL STOCK LASTS
UNTIL 15-6-96

- | | |
|-------------------------------------|--------------|
| (1) All Konig Video Repair Kits | 15% off |
| (our catalogue prices) | |
| (2) Video head puller | £499 each |
| (3) VHS Motorised Adaptor | £1399 each |
| (4) Set of Allen keys | £110 each |
| (5) Sony KSS210A CD Pick Up | £1599 each ★ |
| (6) Baby - 10 Regulator | £1499 each |
| (7) Ferguson Green Spot Lopt | £1099 each |
| (8) Tea 2018A x 3PCs | £399 for 3 |
| (9) UC 3842 x 3 PCs | £399 each |
| (10) BU 208A-TOSH x 2PCs | £450 for 2 |
| (11) BUT11AF-PHIL x 3PCs | £195 for 3 |
| (12) Hitachi: VTII Pinch Roller x 2 | £300 for 2 |
| (13) Philips Remote RC 300 | £515 each |

VALID UP TO 15/6/96

FUSIBLE RESISTORS

QUARTER: WATT	320p/pack
HALF: WATT	399p/pack
ONE: WATT	425p/pack
10 per pack	

SATELLITE PARTS

PACE: SS9K Chopper TXT	799p
PACE: SS9K 47UF/400V	299p
PACE: SS9K 4R7 2W Plg	095p
PACE: PRD800 10R 2W Non/Spiral	085p
PACE: PRD800 1R 1W Non/Spiral	065p
PACE: PRD800 Chopper TXT	899p

POWER SUPPLY REPAIR KITS

PANASONIC NV-730

VIDEO HEAD ONLY

£14.00 Valid up to 15.6.1996

ELECTROLYTIC CAPACITORS

250 VOLTS

1µf	5/100p
4.7µf	5/150p
10µf	5/170p
22µf	each 040p
33µf	each 056p
47µf	each 065p
100µf	each 128p

400 VOLTS

1µf	5/110p
2.2µf	5/110p
4.7µf	5/110p
10µf	each 070p
47µf	each 140p

350 VOLTS

4.7µf	5/100p
10µf	5/060p
22µf	each 070p
33µf	each 070p
47µf	each 095p
100µf	each 100p

HIGH TEMP SUITABLE FOR PANASONIC

10000/16v	each
22000uf/16v	each 399p
6800uf/35v	each 315p
10000uf/35v	each 399p
2200uf/63v	each 299p
4700uf/63v	each 435p
1000/100v	each 350p
2200/100v	each 535p
220/200v	each 240p
330/200v	each 299p
470uf/200v	each 365p
10000uf/200v	each 679p
68uf/400v	each 299p
100uf/400v	each 315p
220uf/400v	each 599p
330uf/400v	each 775p

105° ELECTROLYTIC RADIAL CAPACITORS IN STOCK

RA100 DESOLDERING STATION PLEASE RING FOR DETAILS

BEST BUY
SONY CD LASER PICK UP:
KSS210a only
£15.99 each

DONT FORGET

JJ's IDLER TYRES

Saves £'s £'s £=pounds



Please phone us for the types not listed. Please add 60p post & packing and then add 17.5% VAT to the total. Callers by appointment only.

J.J. COMPONENTS

63 THE CHASE, EDGWARE,
MIDDX. HA8 5DN, ENGLAND

Tel/Fax: 081-952 4641

Hotline No: 081-381 1700

Free fax orderline 0800 318498